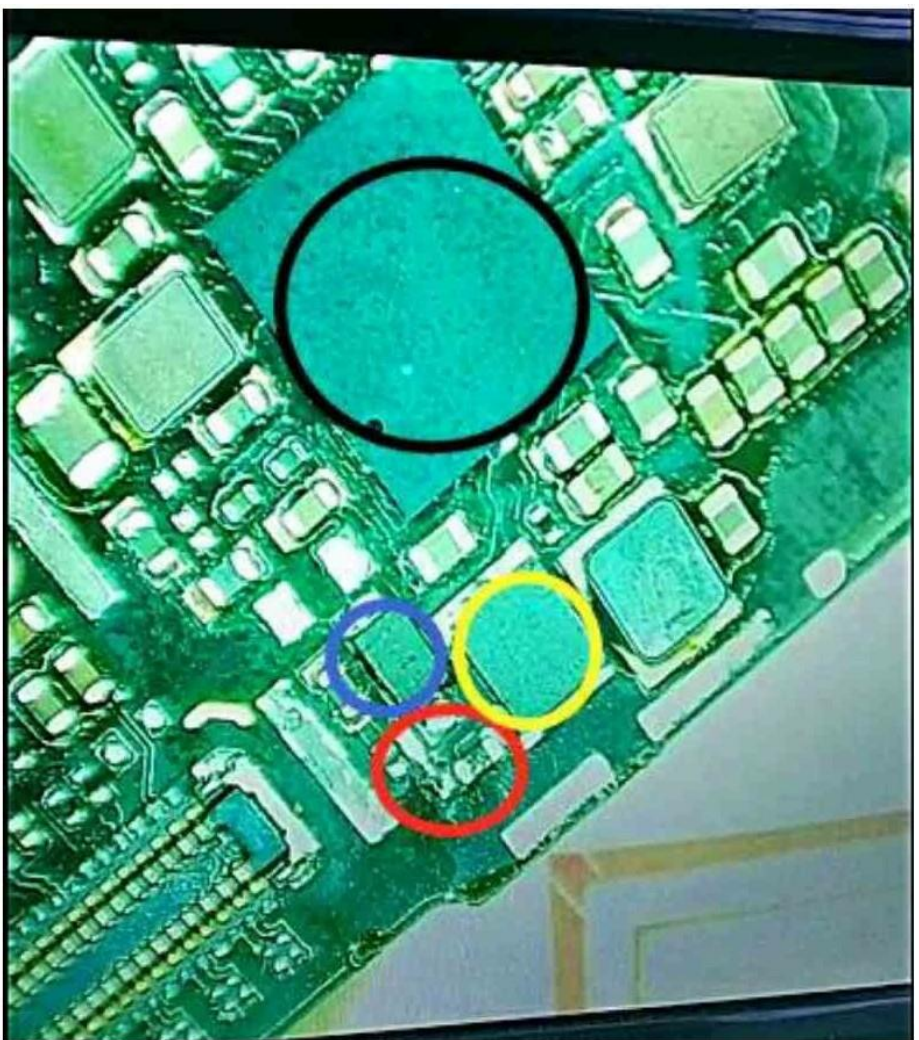


Redmi notes backlight is not on.


Fault performance: display without light.

Maintenance process: the lamp control part is found through the principle, and it is observed that the parts at the red mark are broken. According to the principle Jump wire short-circuit, this line is Short circuit, and then the coil at the yellow mark is burned and replaced.




Burn the diode at the blue mark again; Replace;

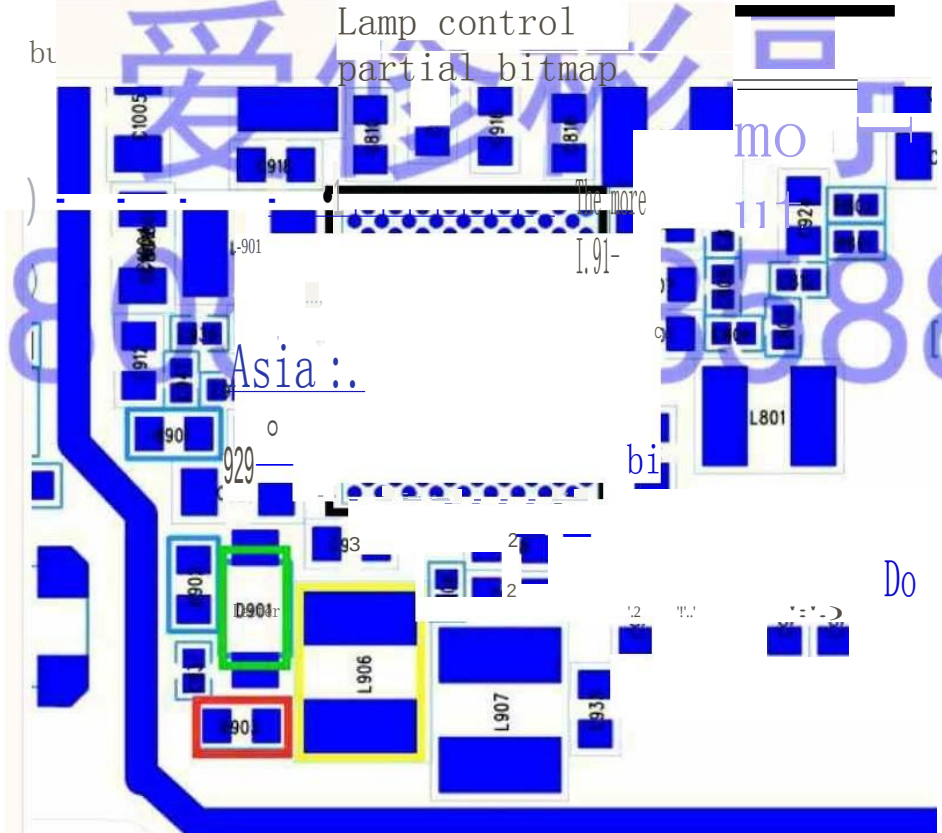Finally, the power supply at the black mark was



Finally, the coil, diode and power supply are replaced in turn, and the fault is solved! Jiaocheng Kannian

Lamp control part schematic

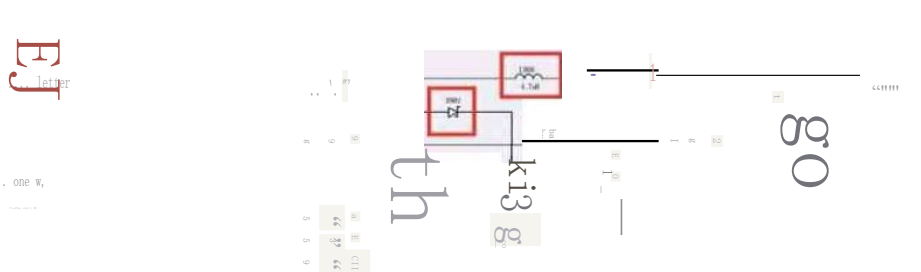

Principle analysis: This case is a chain reaction caused by Fall hard-led light control circuit Short circuit, and then maintenance. However, no matter how complicated it is, the light control circuit is still a coil, diode and light control. The light control of this model is an integrated power supply, which also integrates charging, display and flashing lights. With so much work in charge, the power supply is easily damaged.