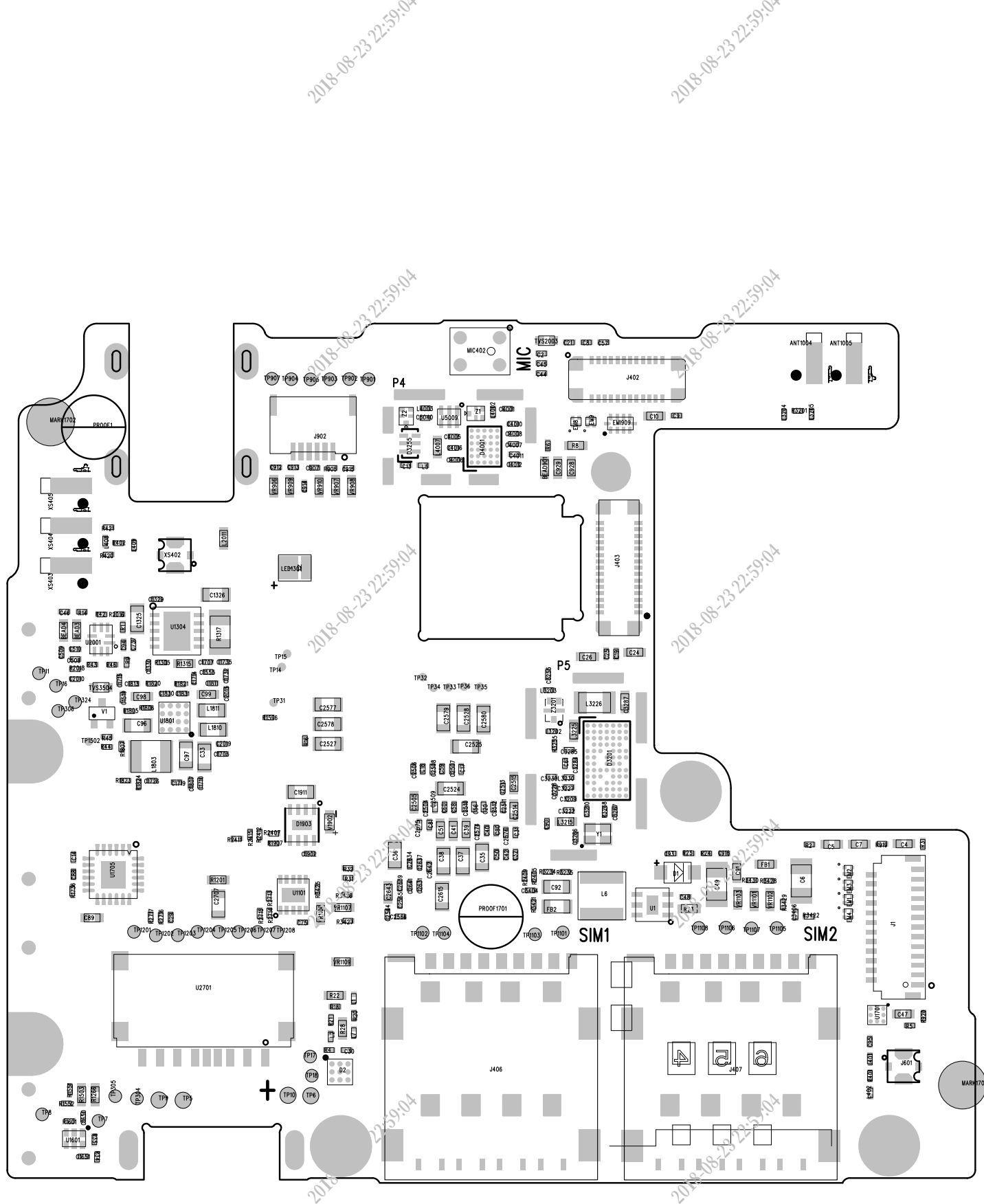




2018-08-23 22:59:04

2018-08-23 22:59:04

L1860_SP_HS_01

01_INDEX01	20_AUDIO&Sub
02_RF BLOCK	21_LC1860_RF&HSL
04_ANT&SWITCH	22_LC1860_PHY
05_PA(SKY77754)	23_LC1860_GPIO1
07_PRIMARY PATH	24_LC1860_GPIO2
09_SECONDARY PATH	25_LC1860_PWR1
10_IRIS411:CLK&DCDC	26_LC1860_PWR2
11_IRIS411:RFIC	27_MEMORY_EMMC&TF
12_GSM1:SWITCH&PA	28_CTP&LCD
13_GAM1 RX FILTER	29_CAMERA
14_GSM1:304&CLK	31_NFC_NM
15_LC1160_CHARGR&CTL	32_BT&WIFI&FM_BCM
16_LC1160_BUCK	33_GPS_BCM
17_LC1160_LDO	34_SIM_CARD
18_LC1160_CODEC	35_KEYPAD&Logic
19_BAT&USB	36_TEST&MARK

818900000331 26007_1_10
DDR3: EDF816423PF-GD-F
eMMC: SDINSD2-8G

2018-08-23 22:59:04


2018-08-23 22:59:04

2018-08-23 22:59:04

2018-08-23 22:59:04

2018-08-23 22:59:04



2018-08-23 22:59:04

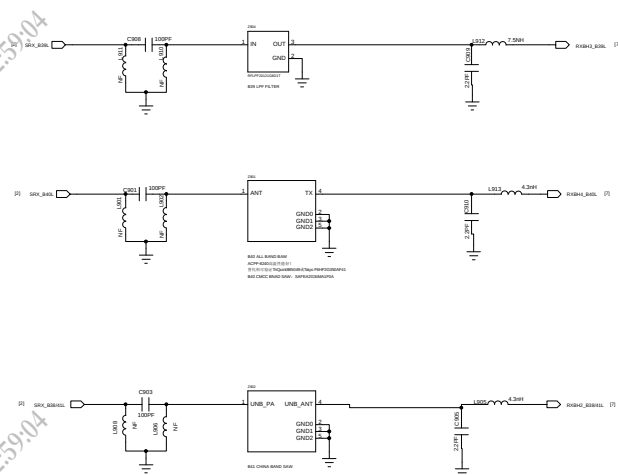


TITLE:			REV:	
DOCUMENT NO.:	Q9_SECONDARY_PATH		SIZED:	A1
DEPARTMENT:	Hardware DEPT.			
COMPANY:	WINGTECH			
DESIGNER:	Last Saved Date:	2015/1/9	SHEET:	5 OF 28




2018-08-23 22:59:04

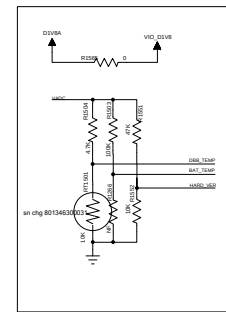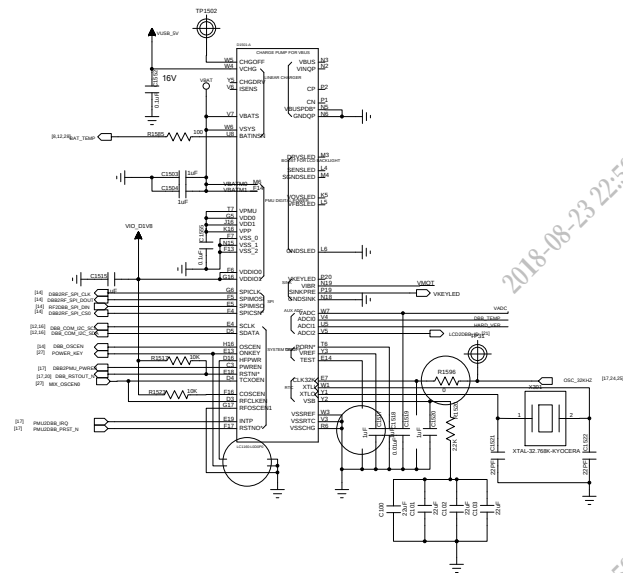


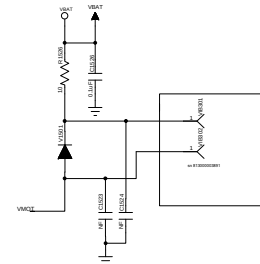
HARD_VER: M10=10K/M11=15K/M20=24K/M21=33K






**WINGTECH**

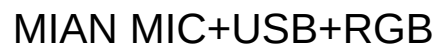



Handset Microphone 1

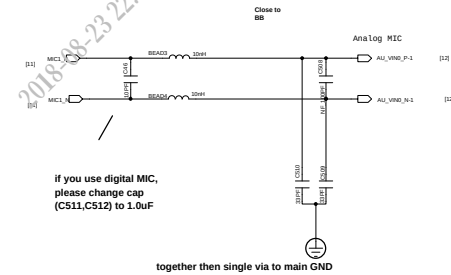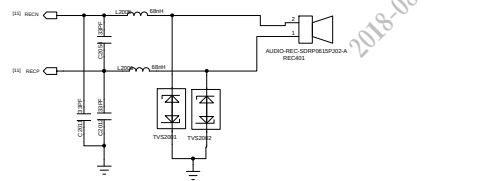


Handset Microphone 2-1

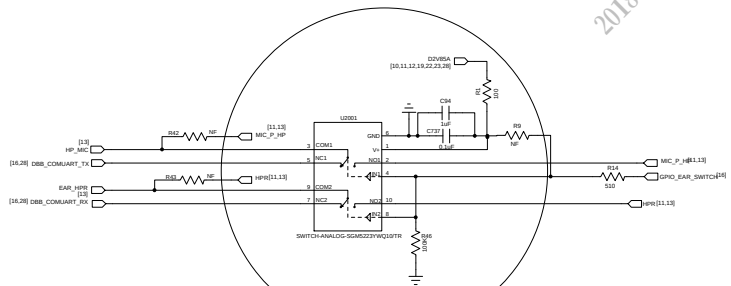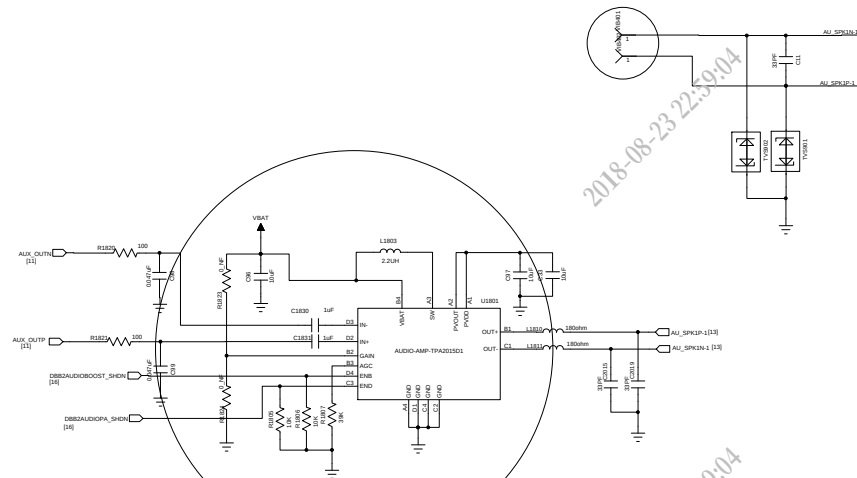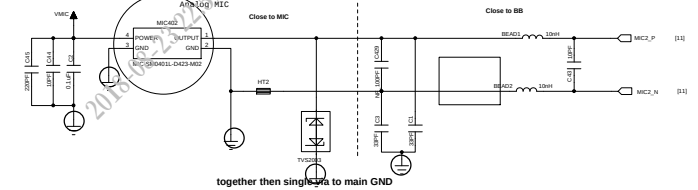

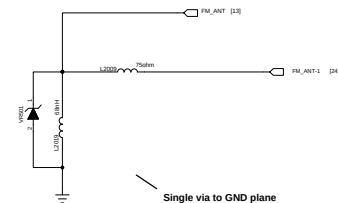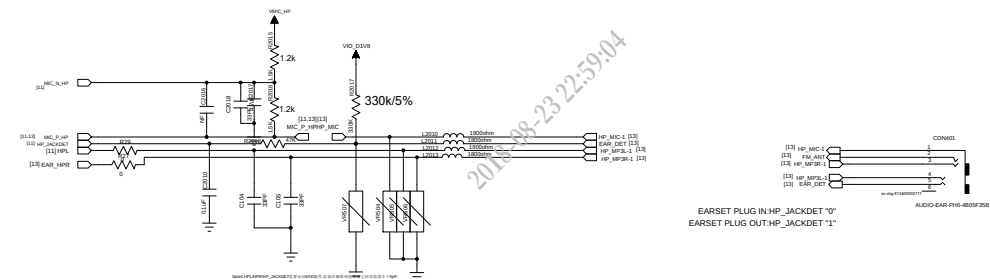IN=0, COM Connected to NC;
IN=1, COM Connected to NO;



TITLE	REV
DOCUMENT NO. 20_AUDIO	SIZED A1
DEPARTMENT Hardware DEPT.	
COMPANY	
DESIGNER	Link Saved Date 2015/1/9
SHEET 13	OF 28

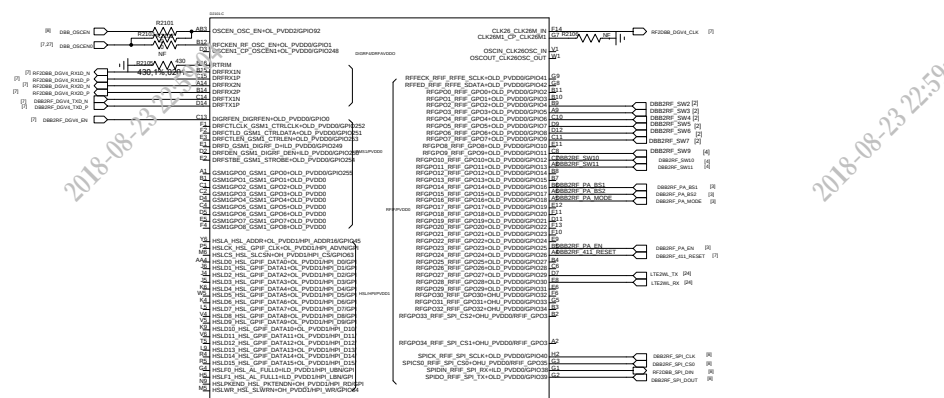


2018-08-23 22:59:04

2018-08-23 22:59:04

2018-08-23 22:59:04


2018-08-23 22:59:04

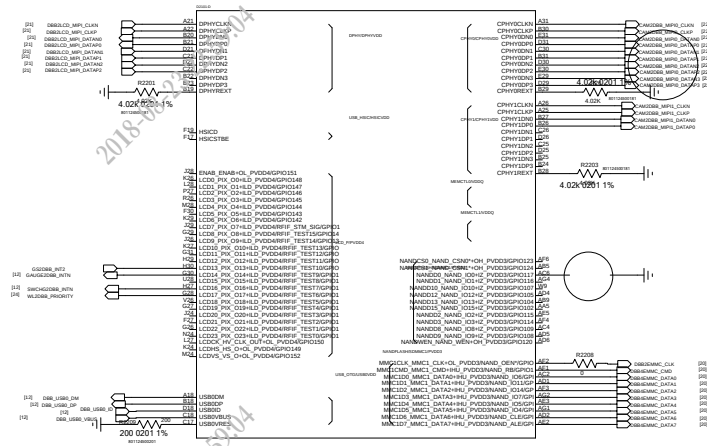



2018-08-23 22:59:04


2018-08-23 22:59:04


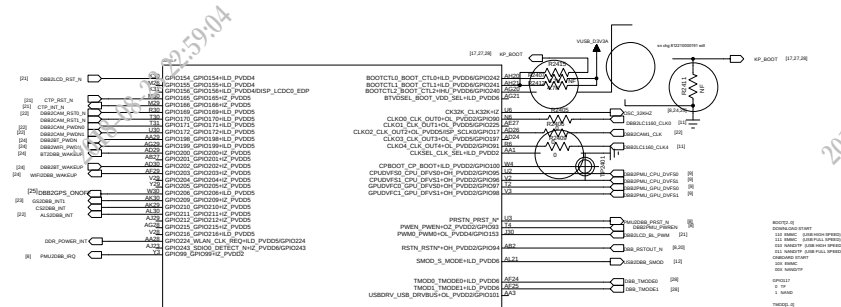


2018-08-23 22:59:04

2018-08-23 22:59:04




2018-08-23 22:59:04

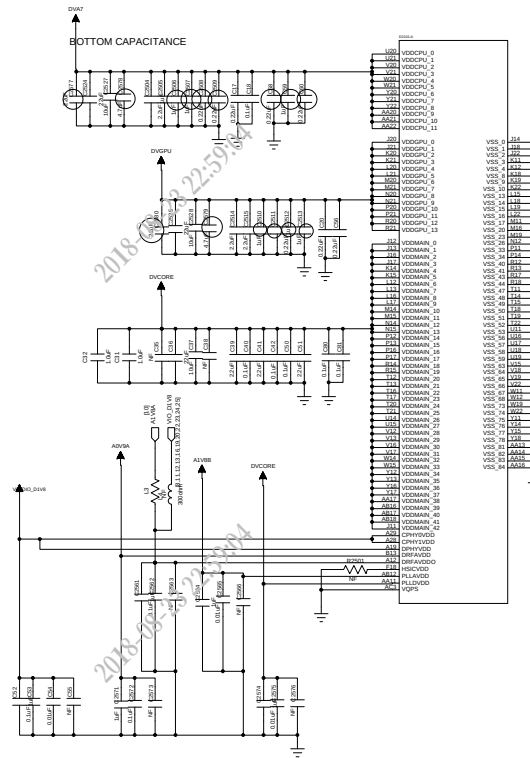

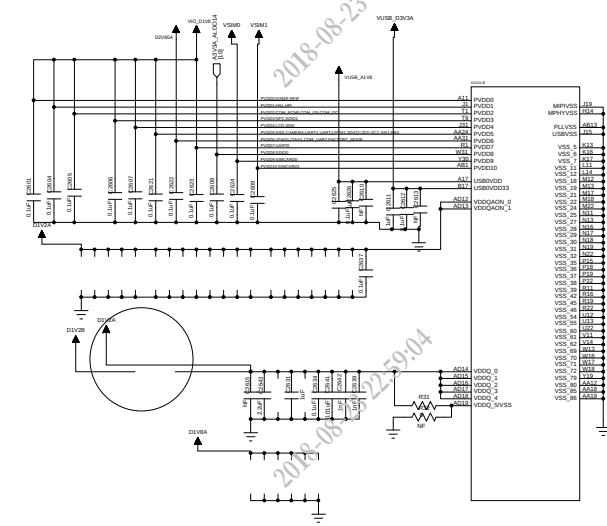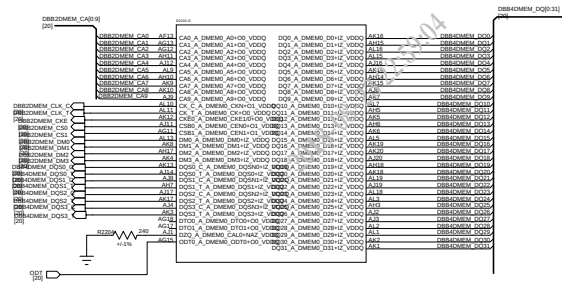



The schematic diagram illustrates the input stage of the 741 op-amp. It features a differential pair of NMOS transistors, M_{N1} and M_{N2} , with their sources connected to a common tail current source M_{N3} . The gates of M_{N1} and M_{N2} are biased by a PMOS network consisting of M_{P1} and M_{P2} . The output is taken from the drains of M_{N1} and M_{N2} , which are loaded with a PMOS network consisting of M_{P3} and M_{P4} . A compensation capacitor C_C is connected between the output node and ground. The input signal V_{IN} is applied to the gates of M_{N1} and M_{N2} . The output voltage V_{OUT} is taken from the output node. The schematic also shows the connection to the V_{DD} and V_{SS} supply rails.

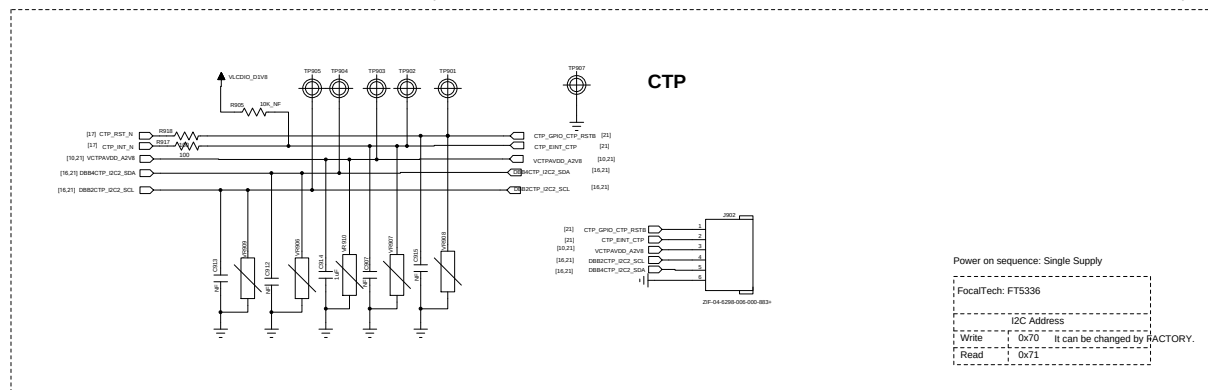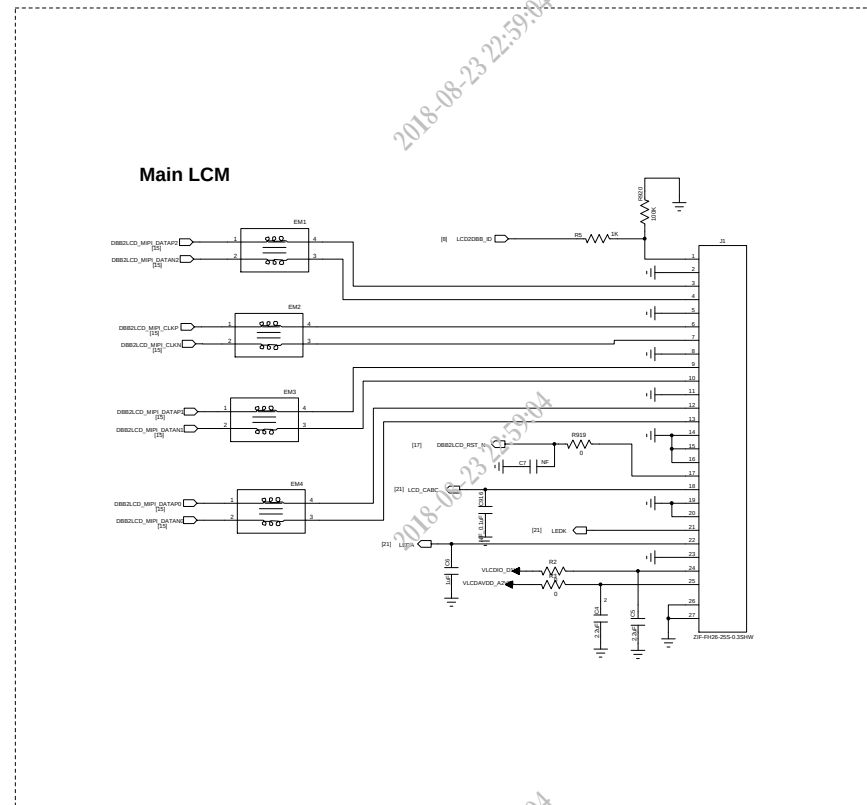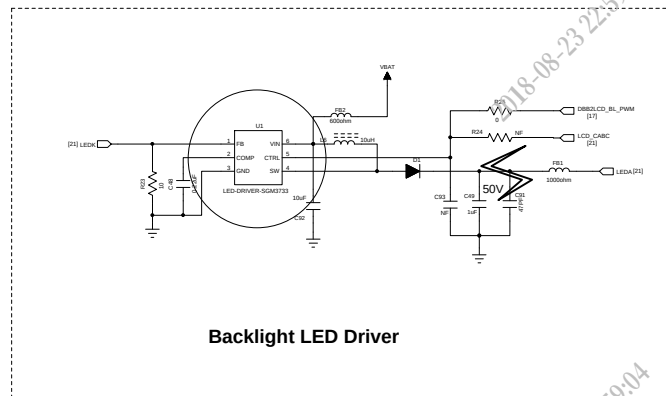

LCD&CTP


Power on sequence: Single Supply

FocalTech: FT5336
 I2C Address
 Write 0x70 It can be changed by FACTORY.
 Read 0x71

TITLE	REV:
DOCUMENT NO. 28_CTP&LCD	SIZED: A1
DEPARTMENT: Hardware DEPT.	
COMPANY: WINTECH	
DESIGNER:	Link Saved Date: 2015/1/9 SHEET: 21 OF 28

2018-08-23 22:59:04

2018-08-23 22:59:04

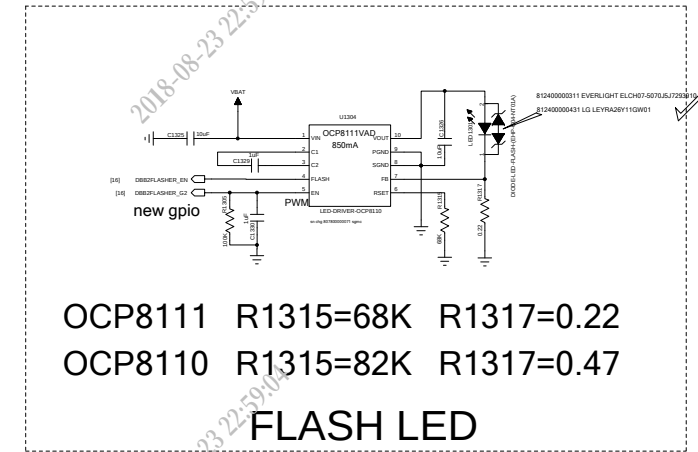


2018-08-23 22:59:04

Sub Camera


FRONT_camera+LP Sensor

light sensor 0x90 Write (STK3171)
light sensor 0x46 Write (LTR-558ALS)

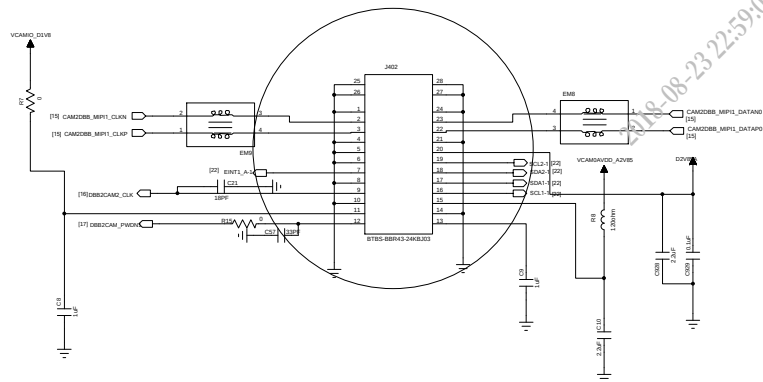Main camera / Sub Camera share power domain design
should double check the voltage level is compatible



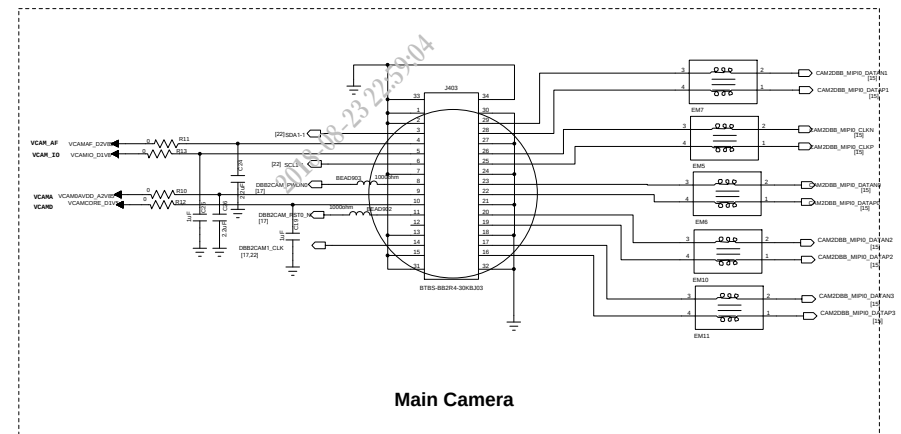Main Camera / Sub Camera share power domain design
should double check the voltage level is compatible



TITLE	29_CAMERA	REV	A1
DOCUMENT NO.	29_CAMERA	SIZED	A1
DEPARTMENT	Hardware DEPT.		
COMPANY	WINTECH		
DESIGNER	Link Server Date	2015/1/9	SHEET 22 OF 28


2018-08-23 22:59:04

2018-08-23 22:59:04

2018-08-23 22:59:04


2018-08-23 22:59:04

M-Sensor

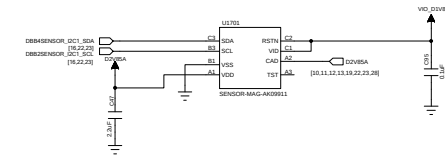


AKM: AK09911	
I2C Address@CAD=0	
Write	0x18
Read	0x19
I2C Address@CAD=1	
Write	0x1A
Read	0x1B

Gyroscope

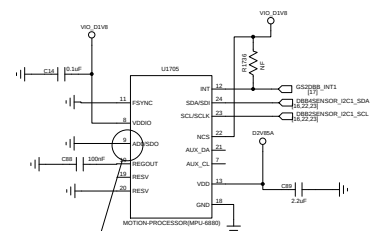

AD0=0 7b1101000 0x68
AD0=1 7b1101001 0x69

InvenSense: MPU6880	
I2C Address@AD0=0	
Write	0xD0
Read	0xD1
I2C Address@AD0=1	
Write	0xD2
Read	0xD3

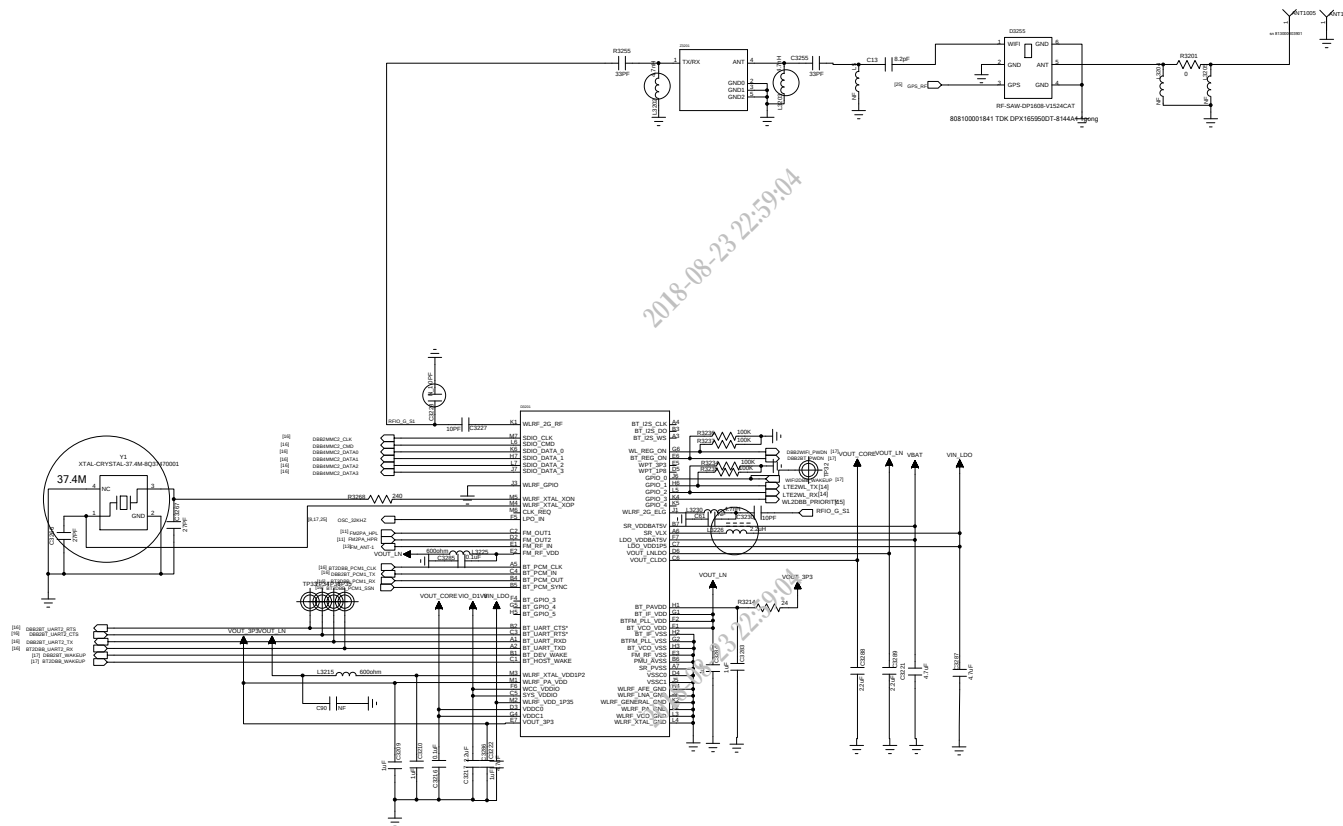



TITLE:			REV:	
DOCUMENT NO.:	_35_KEYPAD&LOGIC		SIZED:	A1
DEPARTMENT:	Hardware DEPT.			
COMPANY:	WINGTECH			
DESIGNER:	Last Saved Date	2015/9/9	SHEET	27 OF 28



TEST_PINS01

TITLE		REV:
DOCUMENT NO.: , 36_TEST&MARK		SIZED: A1
DEPARTMENT: Hardware DEPT.		
COMPANY: 		
DESIGNER:	Last Saved Date: 2015/1/9	SHEET: 28 OF 28